

[By OnlineInterviewQuestions.com](http://OnlineInterviewQuestions.com)

[Circuit Theorems and Conversions MCQ](#)

Take Circuit Theorems and Conversions MCQ Test to Test Your Knowledge

Practice here the best **Circuit Theorem and Conversion MCQ Questions** that test your basic knowledge of circuit theorems and conversions. There are 20+ multiple choice questions in this MCQ test. You have to choose the correct answer for all the questions. Apart from this, you can also download here **Circuit Theorem and Conversions MCQ PDF** completely free of cost.

Q1. Conversions between delta-type and wye-type circuit arrangements are useful in certain specialized applications.

- **A. True**
- B. False

Q2. What is the values for an equivalent current source. When A certain voltage source has the values $V_S = 30 \text{ V}$ and $R_S = 6 \text{ ?}$

- **A. 5 A, 6 Ω ;**
- B. 30 A, 6 Ω ;
- C. 5 A, 30 Ω ;
- D. 30 A, 5 Ω ;

Q3. An ideal current source has zero internal resistance.

- A. True
- **B. False**

Q4. A certain current source has the values $I_S = 4 \mu\text{A}$ and $R_S = 1.2 \text{ M}$. The values for an equivalent voltage source are ____.

- A. 4.8 V, 1.2 M Ω ;
- **B. 1 V, 1.2 M Ω ;**

- C. 4.8 V, 4.8 M Ω ;
- **D. 4.8 V, 1.2 M Ω ;**

Q5. A transistor is basically ____.

- **A. a current amplifier**
- B. a voltage source
- C. power
- D. None of the above

Q6. A 120 V voltage source has a source resistance R_S , of 60 Ω ; . The equivalent current source is ____.

- **A. 2 A**
- B. 4 A
- C. 200 mA
- D. 400 mA

Q7. A 120 Ω load is connected across an ideal voltage source with $V_S = 12$ V. The voltage across the load is ____.

- A. 0 V
- B. 120 V
- **C. 12 V**
- D. None of the above

Q8. You cannot convert a voltage source to an equivalent current source, or vice versa.

- **A. False**
- B. True

Q9. Some circuits require more than one voltage or current source.

- **A. True**
- B. False

Q10. An ideal current source has ___ in parallel with the source.

- **A. an infinite output impedance**
- B. zero internal resistance
- C. zero internal impedance
- D. None of the above

Q11. What is Norton's equivalent current?

- **A. The current source present in the Norton's equivalent circuit is called as Norton's equivalent current.**
- B. The current source present in the circuit is called as Norton's equivalent current.
- C. The voltage source present in the Norton's equivalent circuit is called as Norton's equivalent current.
- D. All of the above

Q12. A practical current source has a finite internal resistance.

- **A. True**
- B. False

Q13. A practical voltage source has a nonzero internal resistance.

- **A. True**
- B. False

Q14. The Thevenin-equivalent voltage is the voltage at the output terminals of the original circuit.

- **A. True**
- B. False

Q15. A certain voltage source has the values $V_S = 30 \text{ V}$ and $R_S = 6 \text{ } \Omega$. The values for an equivalent current source are ___.

- **A. 5 A, 6 Ω**
- B. 30 A, 6 Ω

- C. 5 A, 30 ?
- D. 30 A, 5 ?

Q16. A 2 ? RL is connected across a voltage source, VS, of 110 V. The source's internal resistance is 24 ?. What is the output voltage across the load?

- **A. 8.5 V**
- B. 85 V
- C. 0 V
- D. 110 V

Q17. The current source is converted into the equivalent voltage source:

- **A. $V_S = I_S R_S$**
- B. $V_S = I_S / R_S$
- C. $V_S^2 = I_S R_S$
- D. None of the above

Q18. Superposition works for voltage and current but not power.

- **A. True**
- B. False

Q19. The superposition theorem is applicable to:

- A. linear, non-linear and time variant responses
- B. linear and non-linear resistors only
- **C. linear responses only**
- D. none of the above

Q20. A voltage source having an open-circuit voltage of 100 V and internal resistance of 50 ? is equivalent to a current source:

- **A. 2 A in parallel with 50 ?**
- B. 2 A with 50 ? in series
- C. 0.5 A in parallel with 50 ?
- D. A in parallel with 100 ?